

# Discrete Mathematics

CS204: Spring, 2008

**Jong C. Park**

**Computer Science Department**

**KAIST**

## Today's Topics

Combinatorial Circuits

Properties of Combinatorial Circuits

Boolean Algebras

Boolean Functions and Synthesis of Circuits

Applications

# **BOOLEAN ALGEBRAS AND COMBINATORIAL CIRCUITS**

# Combinatorial Circuits

- Definition

- An **AND gate** receives inputs  $x_1$  and  $x_2$ , where  $x_1$  and  $x_2$  are bits, and produces output denoted  $x_1 \wedge x_2$ , where  $x_1 \wedge x_2 = 1$  if  $x_1 = 1$  and  $x_2 = 1$ , 0 otherwise.
- An **OR gate** receives inputs  $x_1$  and  $x_2$ , where  $x_1$  and  $x_2$  are bits, and produces output denoted  $x_1 \vee x_2$ , where  $x_1 \vee x_2 = 1$  if  $x_1 = 1$  or  $x_2 = 1$ , 0 otherwise.
- A **NOT gate** (or **inverter**) receive input  $x$ , where  $x$  is a bit, and produces output denoted  $\sim x$ , where  $\sim x = 1$  if  $x = 0$ , 0 if  $x = 1$ .

# Combinatorial Circuits

- Note
  - The logic table of a combinatorial circuit lists all possible inputs together with the resulting outputs.
- Examples
  - logic tables for the basic AND, OR, and NOT circuits
  - the combinatorial circuit in Figure 11.1.4
  - the non-combinatorial circuit in Figure 11.1.6
  - the interconnected combinatorial circuit in Figure 11.1.7

# Combinatorial Circuits

- Definition
  - Boolean expressions in the symbols  $x_1, \dots, x_n$  are defined recursively as follows.
    - $0, 1, x_1, \dots, x_n$  are Boolean expressions.
    - If  $X_1$  and  $X_2$  are Boolean expressions, then (a)  $(X_1)$ , (b)  $\sim X_1$ , (c)  $X_1 \vee X_2$ , (d)  $X_1 \wedge X_2$  are Boolean expressions.
  - If  $X$  is a Boolean expression in the symbols  $x_1, \dots, x_n$ , we sometimes write  $X = X(x_1, \dots, x_n)$ .
  - Either symbol  $x$  or  $\sim x$  is called a **literal**.

# Combinatorial Circuits

- Examples
  - Computing the value of a Boolean expression
  - Finding the combinatorial circuit corresponding to the Boolean expression  $(x_1 \wedge (\sim x_2 \vee x_3)) \vee x_2$

# Properties of Combinatorial Circuits

- Theorem

- If  $\wedge$ ,  $\vee$ , and  $\sim$  are as in the previous definitions, then the following properties hold, where  $Z_2 = \{0, 1\}$ .

- (a) Associative laws

- $(a \vee b) \vee c = a \vee (b \vee c)$

- $(a \wedge b) \wedge c = a \wedge (b \wedge c)$  for all  $a, b, c \in Z_2$ .

- (b) Commutative laws

- $a \vee b = b \vee a$

- $a \wedge b = b \wedge a$ , for all  $a, b \in Z_2$ .

- (c) Distributive laws

- $a \wedge (b \vee c) = (a \wedge b) \vee (a \wedge c)$

- $a \vee (b \wedge c) = (a \vee b) \wedge (a \vee c)$  for all  $a, b, c \in Z_2$ .

# Properties of Combinatorial Circuits

(d) Identity laws

- $a \vee 0 = a$

- $a \wedge 1 = a$  for all  $a \in Z_2$ .

(e) Complement laws

- $a \vee \sim a = 1$

- $a \wedge \sim a = 0$  for all  $a \in Z_2$ .



# Properties of Combinatorial Circuits

- Definition
  - Let  $X_1 = X_1(x_1, \dots, x_n)$  and  $X_2 = X_2(x_1, \dots, x_n)$  be Boolean expressions.
  - We define  $X_1$  to be **equal** to  $X_2$  and write  $X_1 = X_2$  if  $X_1(a_1, \dots, a_n) = X_2(a_1, \dots, a_n)$  for all  $a_i \in Z_2$ .
- Example
  - Show that  $\sim(x \vee y) = \sim x \wedge \sim y$ .

# Properties of Combinatorial Circuits

- Definition
  - We say that two combinatorial circuits, each having inputs  $x_1, \dots, x_n$  and a single output, are **equivalent** if, whenever the circuits receive the same inputs, they produce the same outputs.
- Example
  - Equivalence of the combinatorial circuits of Figures 11.2.4 and 11.2.5

# Properties of Combinatorial Circuits

- Theorem
  - Let  $C_1$  and  $C_2$  be combinatorial circuits represented, respectively, by the Boolean expressions  $X_1 = X_1(x_1, \dots, x_n)$  and  $X_2 = X_2(x_1, \dots, x_n)$ .
  - Then  $C_1$  and  $C_2$  are equivalent if and only if  $X_1 = X_2$ .

# Boolean Algebras

- Definition

- A **Boolean algebra**  $B$  consists of a set  $S$  containing distinct elements 0 and 1, binary operators  $+$  and  $\cdot$  on  $S$ , and a unary operator  $'$  on  $S$  satisfying the following laws.

- (a) Associative laws

- $(x + y) + z = x + (y + z)$

- $(x \cdot y) \cdot z = x \cdot (y \cdot z)$  for all  $x, y, z \in S$ .

- (b) Commutative laws

- $x + y = y + x, x \cdot y = y \cdot x$  for all  $x, y \in S$ .

- (c) Distributive laws

- $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$

- $x + (y \cdot z) = (x + y) \cdot (x + z)$  for all  $x, y, z \in S$ .

# Boolean Algebras

(d) Identity laws

–  $x + 0 = x, x \cdot 1 = x$  for all  $x \in S$ .

(e) Complement laws

–  $x + x' = 1, x \cdot x' = 0$  for all  $x \in S$ .

– If  $B$  is a Boolean algebra, we write

$$B = (S, +, \cdot, ', 0, 1).$$

- Examples

- $(Z_2, \vee, \wedge, \sim, 0, 1)$

- $(S, \cup, \cap, \sim, \emptyset, U)$ , where  $U$  is a universal set and  $S = P(U)$ , the power set of  $U$ , with the operations  $X + Y = X \cup Y, X \cdot Y = X \cap Y, X' = \sim X$  on  $S$ .

# Boolean Algebras

- Theorem

- In a Boolean algebra, the element  $x'$  of the complement laws is unique. Specifically, if  $x + y = 1$  and  $xy = 0$ , then  $y = x'$ .

- Proof.

- $y = y1$

- $= y(x + x')$

- $= yx + yx'$

- $= xy + yx'$

- $= 0 + yx'$

- $= xx' + yx'$

- $= x'x + x'y$

- $= x'(x + y)$

- $= x'1$

- $= x'$

# Boolean Algebras

- Definition
  - In a Boolean algebra, we call the element  $x'$  the **complement** of  $x$ .

# Boolean Algebras

- Theorem

- Let  $B = (S, +, \cdot, ', 0, 1)$  be a Boolean algebra. The following properties hold.

- (a) Idempotent laws

- $x + x = x, xx = x$  for all  $x \in S$ .

- (b) Bound laws

- $x + 1 = 1, x0 = 0$  for all  $x \in S$ .

- (c) Absorption laws

- $x + xy = x, x(x + y) = x$  for all  $x, y \in S$ .

- (d) Involution law

- $(x)' = x$  for all  $x \in S$ .



# Boolean Algebras

(e) 0 and 1 laws

- $0' = 1$

- $1' = 0$

(f) De Morgan's laws for Boolean algebras

- $(x + y)' = x'y$  for all  $x, y \in S$

- $(xy)' = x' + y'$  for all  $x, y \in S$ .

# Boolean Algebras

- Definition
  - The **dual** of a statement involving Boolean expressions is obtained by replacing 0 by 1, 1 by 0, + by  $\cdot$ , and  $\cdot$  by +.
- Example
  - Determine the dual of  $(x + y)' = x'y'$ .

# Boolean Algebras

- Theorem
  - The dual of a theorem about Boolean algebras is also a theorem.
  - Proof.
    - Suppose that  $T$  is a theorem about Boolean algebras.
    - Then there is a proof  $P$  of  $T$  involving only the definitions of a Boolean algebra.
    - Let  $P'$  be the sequence of statements obtained by replacing every statement in  $P$  by its dual.
    - Then  $P'$  is a proof of the dual of  $T$ .

# Boolean Algebras

- Example

- The dual of

$$(x + x') = x$$

is

$$xx = x.$$

- Recall the proof:

- $x = x + 0$   
 $= x + (xx')$   
 $= (x + x')(x + x)$   
 $= (x + x')1$   
 $= x + x$

- Now the proof:

- $x = x1$   
 $= x(x + x')$   
 $= xx + xx'$   
 $= xx + 0$   
 $= xx.$

# Summary

- Combinatorial Circuits
- Properties of Combinatorial Circuits
- Boolean Algebras
- Boolean Functions and Synthesis of Circuits
- Applications